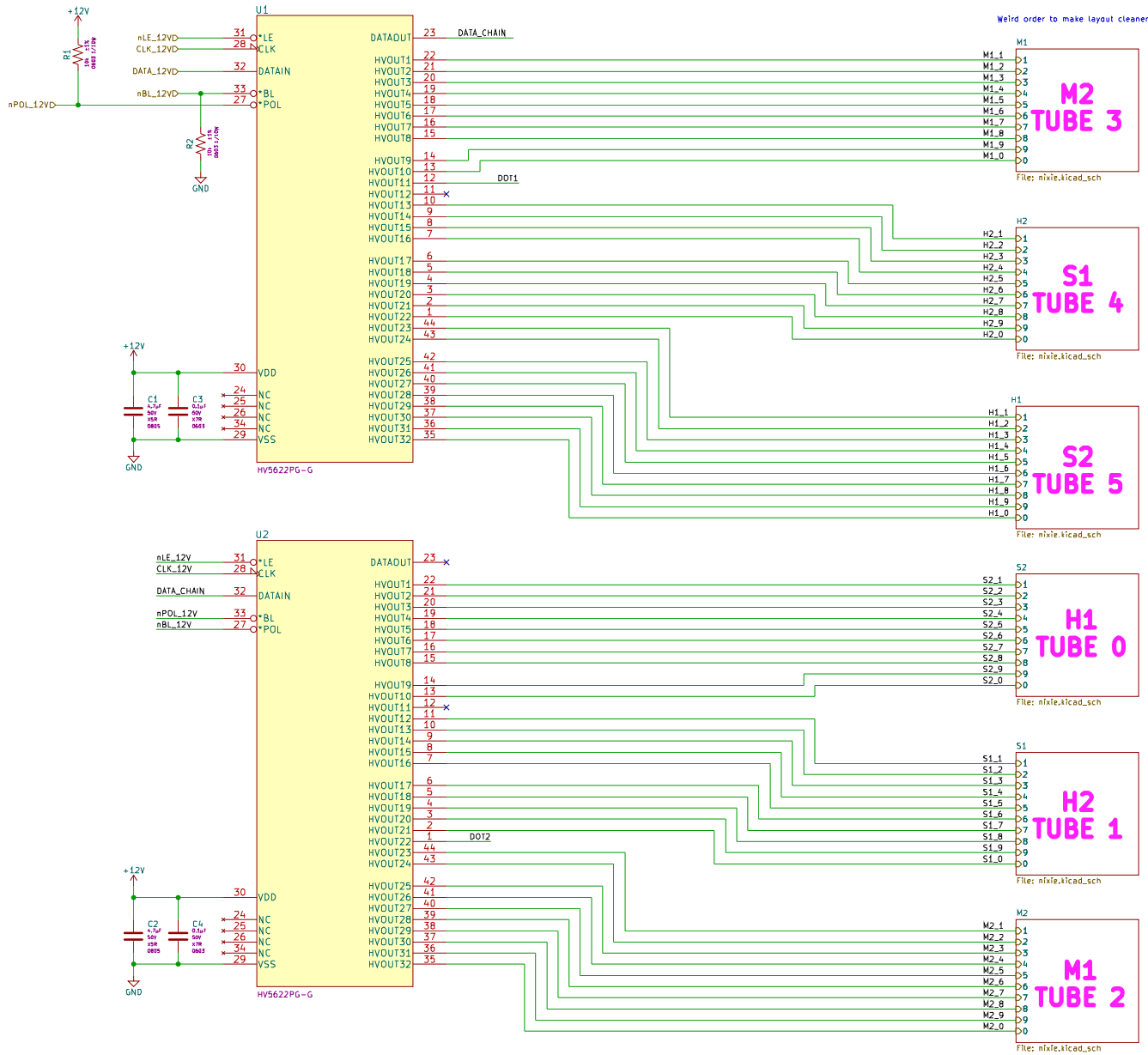


CLK transitions on falling edge
 Transfer of data from the Shift register to the latch occurs when the nLE input is high. (When active low the data is latched and not shown to the output.)
 The data in the latch is stored when nLE is low i.e. outputs are latched (active low)
 nBL LOW sets all outputs off – pulled down to ensure all Nixie's off by default.
 – Can PWM this to dim the Nixies
 nPOL LOW inverts all outputs (keep HI for normal operation)






Also realizing I made a booboo with the layout I put hours on the "left" and seconds on the "right" in layout... but the layout is "looking outward" meaning the order is actually inverted.

H1 == S2
 H2 == S1
 M1 == M2
 M2 == M1
 S1 == H2
 S2 == H1

IN-3 Lamp Spec:
 $60 < V_{ignition} < 90$
 $I_{rated} = 0.8mA$
 $I_{max} = 1mA$

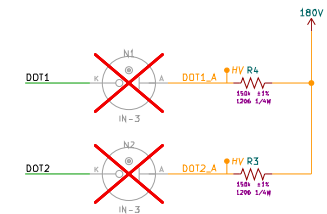
$R_a = (180 - 60) / 0.8mA = 150k\Omega$
 $P_{Ra} = 0.8mA^2 \cdot 150k = 96mW$



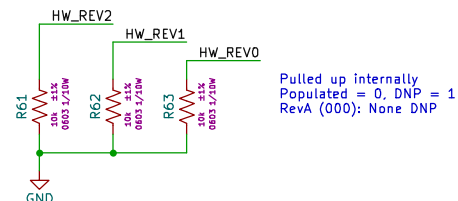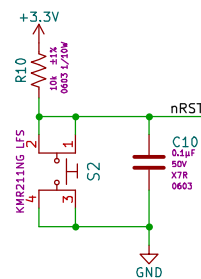


<https://threeneurons.wordpress.com/nixie-power-supply/>
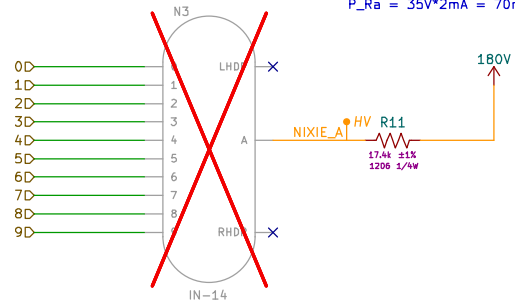
```
Vstrike = 170V
Vmax = 200V
170V < Vsupply = 180V < 200V
Vsustain = 145V
I = 2mA (Shift register has 100mA max shift current, so we're good there)
Ra = (180V-145V)/2mA = 17.5k
P_Ra = 35V*2mA = 70mW
```




<https://threeneurons.wordpress.com/nixie-power-supply/>

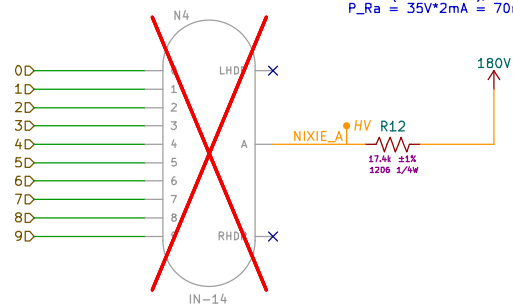$V_{strike} = 170V$
 $V_{max} = 200V$
 $170V < V_{supply} = 180V < 200V$
 $V_{sustain} = 145V$
 $I = 2mA$ (Shift register has 100mA max shift current, so we're good there)
 $R_a = (180V - 145V) / 2mA = 17.5k$
 $P_{Ra} = 35V * 2mA = 70mW$




<https://threeneurons.wordpress.com/nixie-power-supply/>

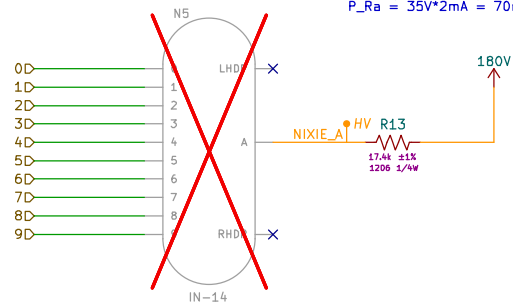$V_{strike} = 170V$
 $V_{max} = 200V$
 $170V < V_{supply} = 180V < 200V$
 $V_{sustain} = 145V$
 $I = 2mA$ (Shift register has 100mA max shift current, so we're good there)
 $R_a = (180V - 145V) / 2mA = 17.5k$
 $P_{Ra} = 35V * 2mA = 70mW$




<https://threeneurons.wordpress.com/nixie-power-supply/>

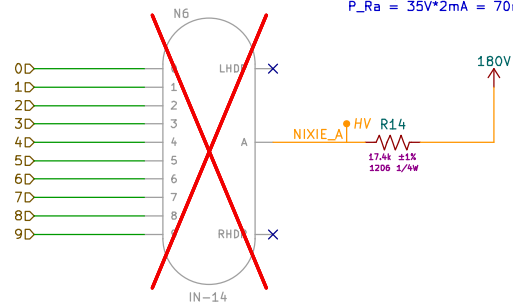$V_{strike} = 170V$
 $V_{max} = 200V$
 $170V < V_{supply} = 180V < 200V$
 $V_{sustain} = 145V$
 $I = 2mA$ (Shift register has 100mA max shift current, so we're good there)
 $R_a = (180V - 145V) / 2mA = 17.5k$
 $P_{Ra} = 35V * 2mA = 70mW$




<https://threeneurons.wordpress.com/nixie-power-supply/>

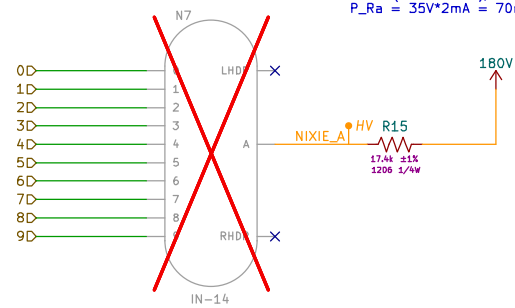
$V_{strike} = 170V$
 $V_{max} = 200V$
 $170V < V_{supply} = 180V < 200V$
 $V_{sustain} = 145V$
 $I = 2mA$ (Shift register has 100mA max shift current, so we're good there)
 $R_a = (180V - 145V) / 2mA = 17.5k$
 $P_{Ra} = 35V * 2mA = 70mW$



<https://threeneurons.wordpress.com/nixie-power-supply/>

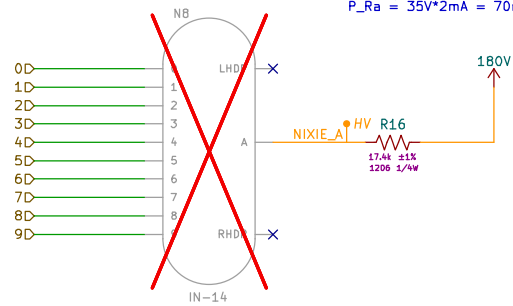
$V_{strike} = 170V$
 $V_{max} = 200V$
 $170V < V_{supply} = 180V < 200V$
 $V_{sustain} = 145V$
 $I = 2mA$ (Shift register has 100mA max shift current, so we're good there)
 $R_a = (180V - 145V) / 2mA = 17.5k$
 $P_{Ra} = 35V * 2mA = 70mW$



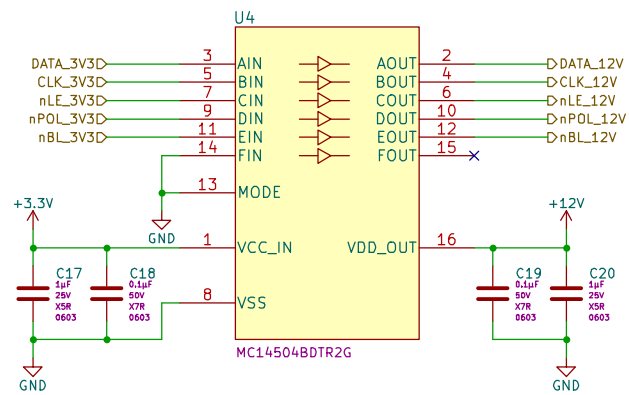


!! Check level shifter power sequencing requirements

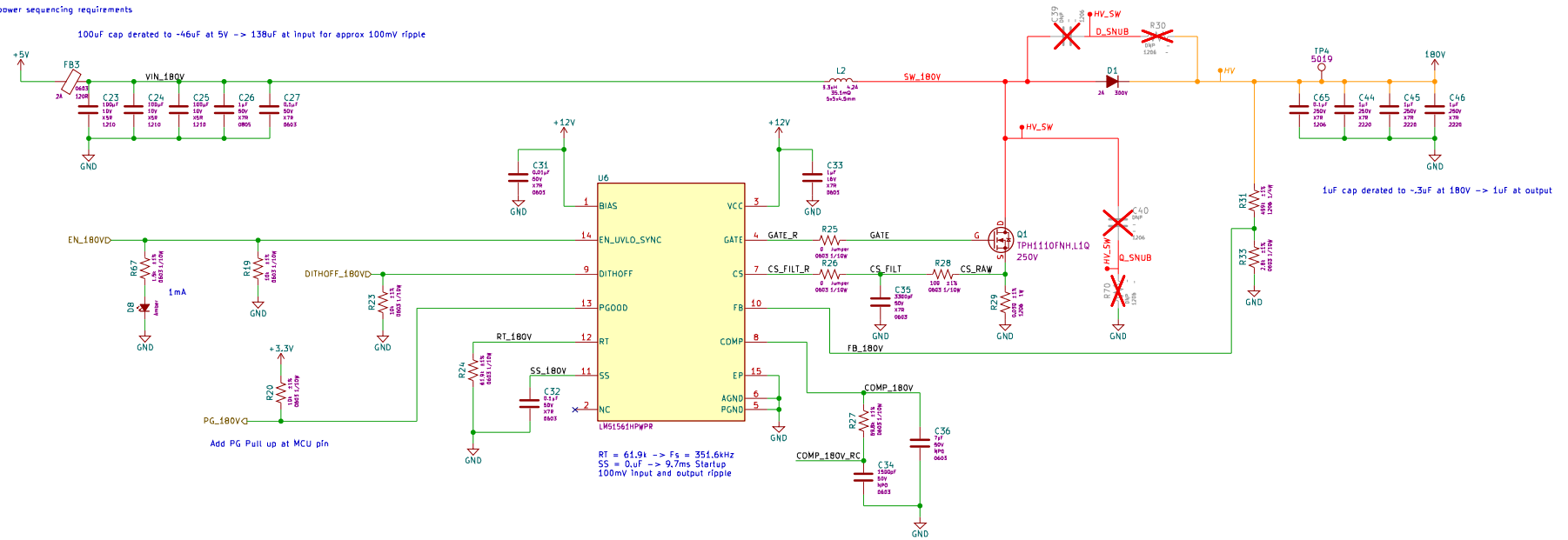100uF cap derated to ~46uF at 5V -> 138uF at Input for approx 100mV ripple




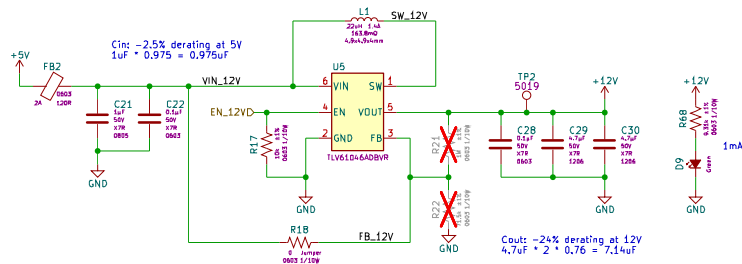R27 and C36 add a low frequency compensation zero at 1.5kHz
C34 adds a high frequency compensation pole at 32.7kHz




FB to VIN defaults to 12V out
Pout_max = 384mW
Vout_ripple = 30mV (PFM), 2.6mV (PWM)
Iout_max = 32mA
Iin_max = 93mA

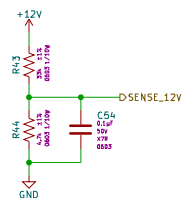
Cout ~24% derating at 12V
4.7uF * 2 * 0.76 = 7.14uF




124.7 mV/V
12V input -> 1.496V at ADC Input
3.3V at ADC Input would need to be a 26.5V Input
Input impedance to ADC is 33k || 4.7k = 4.11k
- This is less than 50k max R_ain of the ADC
fc = 387 Hz
- Place filter cap near MCU pin

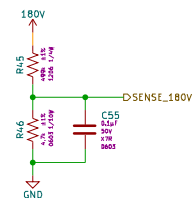

9.33 mV/V
180V input -> 1.6795V at ADC Input
3.3V at ADC Input would need to be a 353V Input.
Input impedance to ADC is 499k || 4.7k = 4.67k
- This is less than 50k max R_ain of the ADC
fc = 342Hz
- Place filter cap near MCU pin

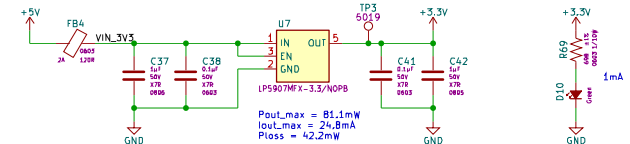

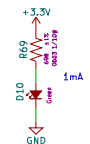Pout_max = 81.1mW
Iout_max = 24.8mA
Ploss = 42.2mW



Rotary Encoder w/Pushbutton

Main user input

